


18.1 Given: $\mathcal{E} = 1.5 \text{ V}$
 $r = 1.0 \Omega$ (internal resistance)

Find: current, I , for a short circuit.

Here: $\mathcal{E} = Ir$

$$\Rightarrow I = \frac{\mathcal{E}}{r} = \frac{1.5 \text{ V}}{1.0 \Omega} = 1.5 \text{ A}$$

$I = 1.5 \text{ A}$

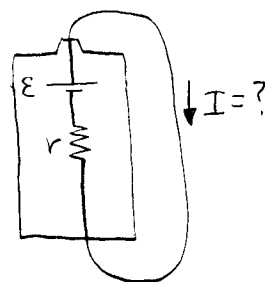


18.3 Given: $\mathcal{E} = 1.5 \text{ V}$
 $r = 0.05 \Omega$
 $I = 0.5 \text{ A}$

Find: terminal voltage of cell

$$V = \mathcal{E} - Ir \quad (\text{terminal voltage of a real battery})$$

$$= 1.5 \text{ V} - (0.5 \text{ A})(0.05 \Omega)$$

$V = 1.475 \text{ V}$

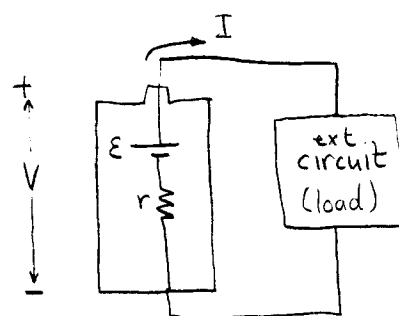

18.7 Given: terminal voltage, $V = 8.85 \text{ V}$
 $r = 0.3 \Omega$
 $I = 0.5 \text{ A}$

Find: power dissipated by the internal resistor.


Power dissipated by any resistor is

$$P = I^2 R \quad (\text{where } I \text{ is the current through } R)$$

So, in this case,

$$P = I^2 r = (0.5 \text{ A})^2 (0.3 \Omega) = 0.075 \text{ W}$$

$P = 75 \text{ mW}$

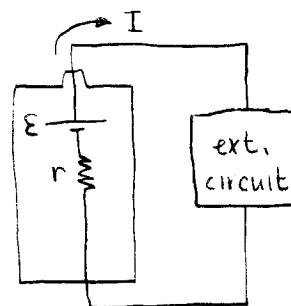

18.9


Given: battery:

$$\mathcal{E} = 9.0 \text{ V}$$

$$r = 0.2 \, \Omega$$

$$(I = 0.882 \text{ A})$$

$$R = 10 \, \Omega$$

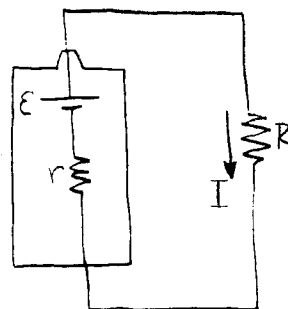

Find: total power dissipated.

Solution:

Power is dissipated by resistors: $P = I^2 R$, in general.

The total power dissipated is the sum of the power dissipated by each resistor:

$$P_{\text{tot}} = I^2 r + I^2 R$$

Since all the circuit elements are in series, the current is the same everywhere. This current is determined by the emf and the total resistance:

$$I = \frac{\mathcal{E}}{R + r} = \frac{(9.0 \text{ V})}{10 \, \Omega + 0.2 \, \Omega} = 0.882 \text{ A} \quad (\text{which was already given})$$

Thus, the total power dissipated is

$$P_{\text{tot}} = I^2 r + I^2 R = I^2 (r + R) = (0.882 \text{ A})^2 (10.2 \, \Omega)$$

$$P_{\text{tot}} = 7.9 \text{ W}$$

Note that this is also equal to the power delivered by the emf:

$$P = VI = \mathcal{E}I = (9.0 \text{ V})(0.882 \text{ A}) = 7.9 \text{ W}$$

Find: terminal voltage of battery.

$$V = \mathcal{E} - Ir = (9.0 \text{ V}) - (0.882 \text{ A})(0.2 \, \Omega)$$

$$V = 8.8 \text{ V}$$


18.21

$$V = 100 \text{ V}$$

5 100W lamps in parallel

0.1 μ

How much current needed?

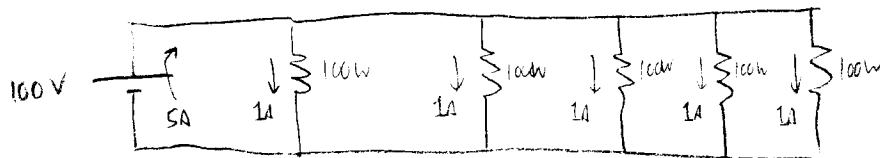

1 lamp:

$$P = VI$$


$$P = 100 \text{ W}$$

$$V = 100 \text{ V}$$

$$\Rightarrow I = 1 \text{ A}$$

$$I_{\text{tot}} = 5 \text{ A}$$

18.57

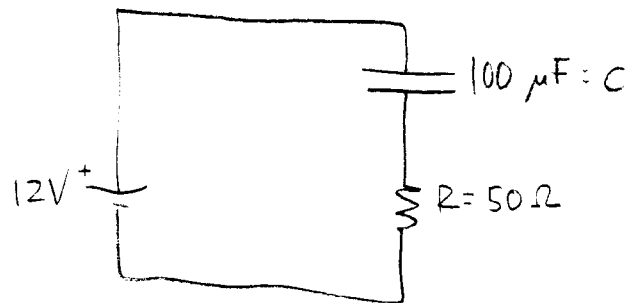

$$\tau = RC$$

$$= (50 \Omega)(100 \times 10^{-6} \text{ F})$$

$$\tau = 0.005 \text{ s} = 5.0 \text{ ms}$$

18.27

Find R_{eq} :

resistors ②, ③, ④, and ⑤
are in parallel with each other:

$$\frac{1}{R_{2345}} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}$$



$$= \frac{1}{2} + \frac{1}{3} + \frac{1}{6} + \frac{1}{1}$$

$$\frac{1}{R_{2345}} = 2 \Rightarrow R_{2345} = \frac{1}{2} \Omega$$

$$R_{eq} = R_1 + R_{2345}$$

$$= 5.0 \Omega + 0.5 \Omega$$

$$R_{eq} = 5.5 \Omega$$

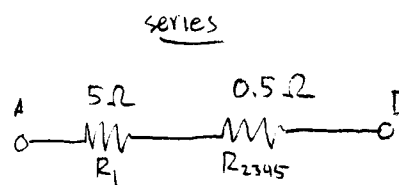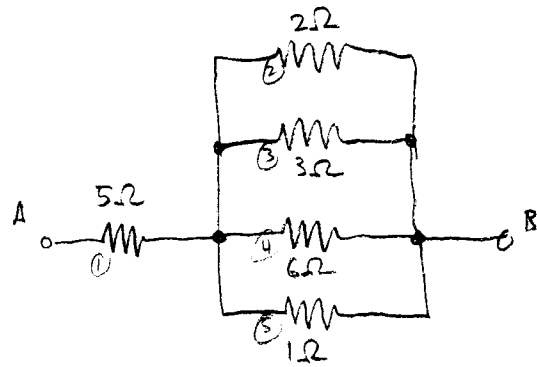


18.61

$$C = 1.0 \mu\text{F}$$

$$R = 2.0 \text{ M}\Omega$$

$$\mathcal{E} = V = 12.0 \text{ V}$$

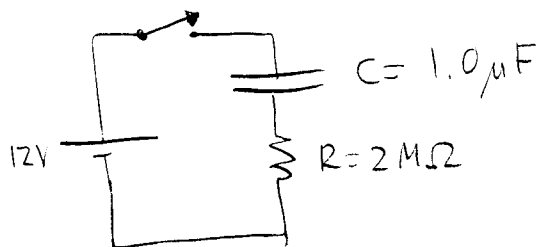

RC

Voltage

$$V @ \tau = RC$$

$$V(t=\tau) = 0.37 V_i$$

$$I = \frac{\mathcal{E}}{R} e^{-t/RC}$$

$$@ t=0 \quad I(t=0) = I_i = \frac{\mathcal{E}}{R} e^{-0} = \frac{\mathcal{E}}{R} = I_i$$

$$I(t) = I_i e^{-t/RC}$$

$$t \text{ when } I(t) = 0.37 I_i ?$$

$$0.37 I_i = I_i e^{-t/RC}$$

$$0.37 = e^{-t/RC}$$

$$\ln 0.37 = -t/RC$$

$$t = -RC \ln 0.37$$

$$= -(2 \times 10^6 \Omega)(1.0 \times 10^{-6} \text{ F}) \ln 0.37$$

$$t = 1.99 \text{ s}$$

$$t = \tau = RC = 2 \text{ s}$$

18.77

Node A:

$$I_1 = I_2 + I_3$$

Loop 1:

$$3I_2 + 3I_2 - 3I_3 = 0$$

Loop 2:

$$3I_3 - 20V + 8I_1 = 0$$

$$I_1 - I_2 - I_3 = 0$$

$$6I_2 - 3I_3 = 0$$

$$8I_1 + 3I_3 = 20$$

$$\begin{Bmatrix} I_1 \\ I_2 \\ I_3 \end{Bmatrix} = \begin{Bmatrix} 2 \\ 2/3 \\ 4/3 \end{Bmatrix} A$$

OR



Note: This is similar to quiz #4, questions 1(a-b)

$$I_1 = \frac{20V}{10\Omega} = 2A \quad (\text{from IV})$$


$$V_{AC} = 2\Omega \times 2A = 4V \quad (\text{from III})$$

$$I_2 = \frac{4V}{6\Omega} = \frac{2}{3}A \quad (\text{from II})$$

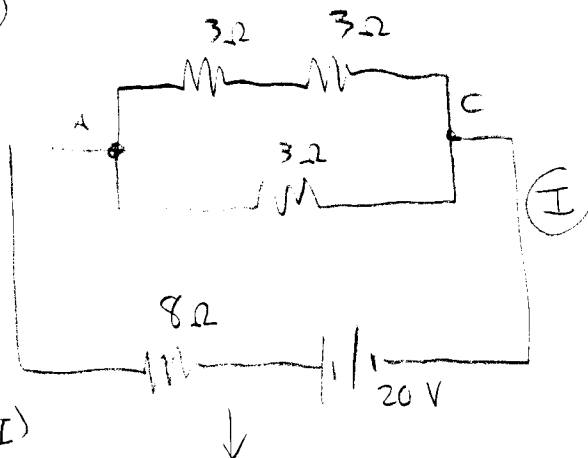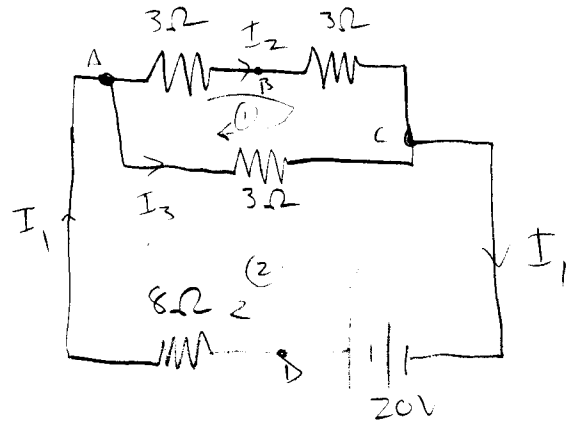
$$I_3 = \frac{4V}{3\Omega} = \frac{4}{3}A$$



(II)

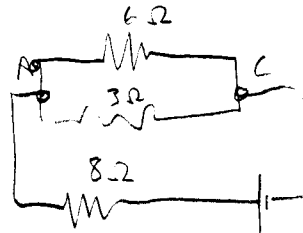

(III)

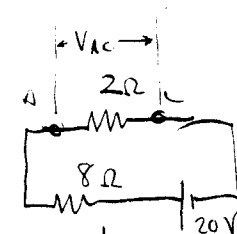

(IV)

