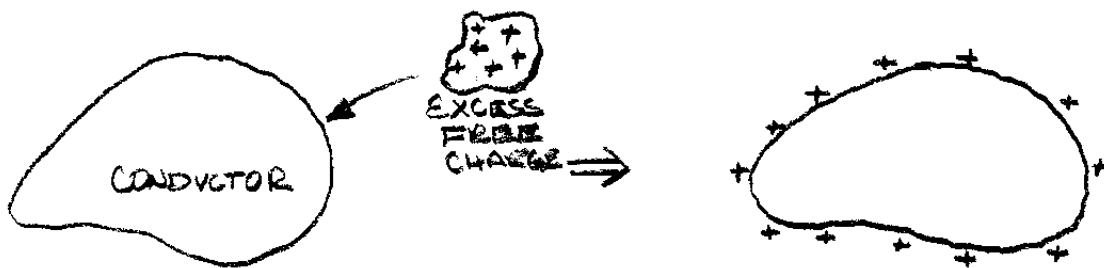


I. CAPACITANCE

(A) DEFINITION OF CAPACITANCE

- CAPACITANCE IS A MEASURE OF AN OBJECT'S ABILITY TO STORE CHARGE

EX! PUT SOME FREE CHARGE ON A CONDUCTOR -



THE CHARGE ARRANGES ITSELF OVER THE SURFACE OF THE CONDUCTOR. THE SURFACE OF THE CONDUCTOR IS AN EQUIPOTENTIAL SURFACE, WITH SOME POTENTIAL V RELATIVE TO A CONVENIENT REFERENCE (SUCH AS $r = \infty$, OR THE SURFACE OF THE EARTH, "GROUND".)

THE CAPACITANCE OF THIS SYSTEM IS DEFINED AS


$$C \equiv \frac{Q}{V} = \frac{(\text{TOTAL CHARGE STORED ON OBJECT})}{(\text{OBJECT'S POTENTIAL})}$$

A TYPICAL UNIT OF CAPACITANCE IS THE FARAD


$$1 \text{ FARAD} = \frac{1 \text{ Coulomb}}{1 \text{ Volt}} = \left(\frac{1 \text{ C}}{1 \text{ V}} \right)$$

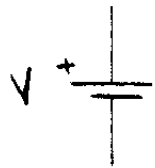(B) IDEAL BATTERY


- HELPFUL TO HAVE SOMETHING THAT CAN MAINTAIN A CONSTANT POTENTIAL ACROSS SOME SYSTEM REGARDLESS OF QUANTITY OF CHARGE DELIVERED TO/FROM SYSTEM. CALL THIS AN IDEAL BATTERY
- SCHEMATIC SYMBOL FOR IDEAL BATTERY



MEANS:

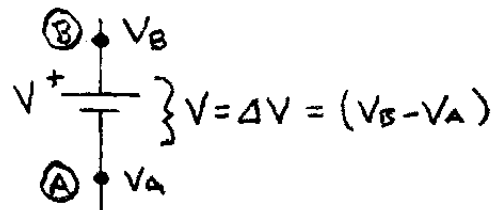


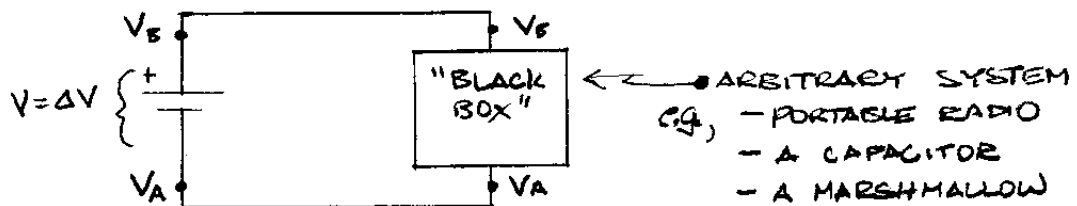OBJECT WHICH MAINTAINS A CONSTANT POTENTIAL DIFFERENCE $V = \Delta V = (V_B - V_A)$ BETWEEN ITS TWO TERMINALS (A) AND (B) REGARDLESS OF WHAT THOSE TERMINALS ARE CONNECTED TO




- NOTE: ITS CUSTOMARY IN ELECTRONICS TO WRITE POTENTIAL DIFFERENCES WITHOUT THE Δ . I.E., $V = \Delta V = V_2 - V_1$ WHERE V_1 IS SOME CONVENIENT REFERENCE POTENTIAL, USUALLY CHOSEN TO BE $V_1 = 0$ AND CALLED "GROUND"

(C) PARALLEL PLATE CAPACITOR

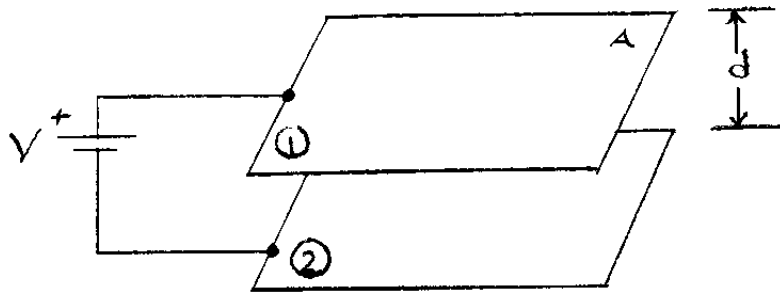

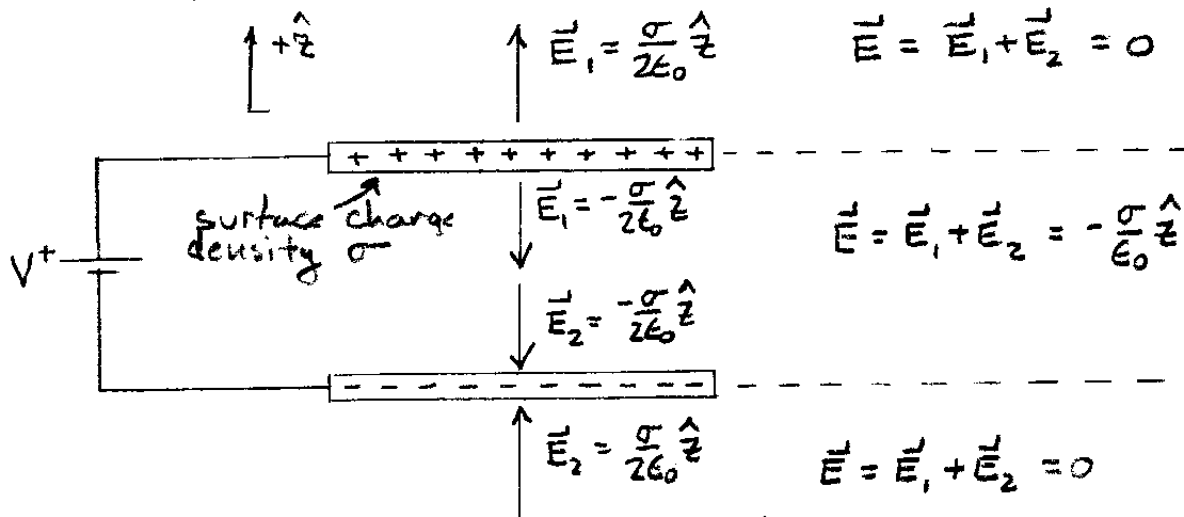- TAKE TWO CONDUCTING SHEETS OF SURFACE AREA A SEPARATED BY SOME DISTANCE d . THIS THING CAN STORE CHARGE. E.G., BY HOOKING PLATES UP TO A BATTERY AS SHOWN ABOVE.



$$V = \Delta V = - \int_{z=0}^{z=d} \vec{E} \cdot d\vec{r} = - \int_{z=0}^{z=d} \left(-\frac{\sigma}{\epsilon_0} \hat{z} \right) (dz \hat{z})$$


$$V = \frac{\sigma}{\epsilon_0} \int_0^d dz = \frac{\sigma}{\epsilon_0} z \Big|_0^d = \frac{\sigma d}{\epsilon_0}$$

$$Q = \sigma A \quad C = Q/V = \frac{\sigma A}{\sigma d / \epsilon_0} = \frac{\epsilon_0 A}{d}$$

$$C = \frac{\epsilon_0 A}{d}$$

CAPACITANCE OF PARALLEL PLATE CAPACITOR

(D) CAPACITANCE OF A SPHERICAL CONDUCTOR

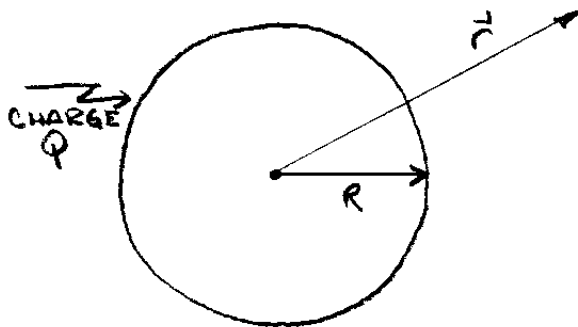

$$C = \frac{Q}{V}$$

$$V = \Delta V = - \int_{\infty}^R \vec{E} \cdot d\vec{r}$$

$$\vec{E} = \frac{1}{4\pi\epsilon_0} \frac{Q}{r^2} \hat{r} \quad d\vec{r} = dr \hat{r}$$

$$\vec{E} \cdot d\vec{r} = \left(\frac{1}{4\pi\epsilon_0} \frac{Q}{r^2} \hat{r} \right) \cdot (dr \hat{r}) = \frac{Q}{4\pi\epsilon_0} \frac{dr}{r^2}$$

$$V = - \frac{Q}{4\pi\epsilon_0} \int_{\infty}^R \frac{dr}{r^2} = \frac{Q}{4\pi\epsilon_0} \frac{1}{r} \Big|_{\infty}^R = \frac{Q}{4\pi\epsilon_0 R}$$

$$C = Q/V = Q / (Q / 4\pi\epsilon_0 R)$$

$$C = 4\pi\epsilon_0 R$$

CAPACITANCE OF SPHERICAL
CONDUCTOR


II, CAPACITORS IN SERIES AND PARALLEL

(A) SCHEMATIC SYMBOL FOR A CAPACITOR



- LOOKS LIKE A PARALLEL PLATE CAPACITOR, BUT JUST MEANS ANYTHING WITH CAPACITANCE. COULD BE A SPHERICAL CAPACITOR, ETC.

(B) CAPACITORS IN PARALLEL

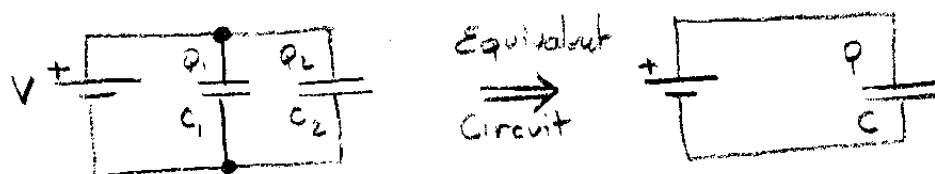

$$Q = Q_1 + Q_2$$


$$CV = C_1 V_1 + C_2 V_2$$

$$\text{but } V = V_1 = V_2$$

$$\Rightarrow \boxed{C = C_1 + C_2}$$

Equivalent Capacitance
of Capacitors in parallel

(C) CAPACITORS IN SERIES

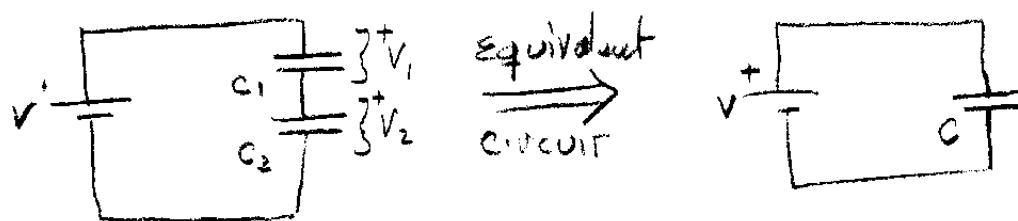

$$V = V_1 + V_2$$

$$\frac{Q}{C} = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$

but $Q = Q_1 = Q_2$

$$\boxed{\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}}$$

Equivalent capacitance
of capacitors in series


- Note: This can also be written

$$C = \frac{C_1 C_2}{C_1 + C_2}$$

and some people prefer to remember this form.
However, it's best to just remember

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

Since, for example

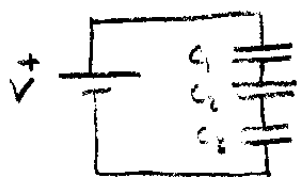

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


(easy to see generalization
to more than two
caps in series)

$$C = \frac{C_1 C_2 C_3}{C_1 C_2 + C_1 C_3 + C_2 C_3}$$

(not easy to see this
as a generalization of
 $C = \frac{C_1 C_2}{C_1 + C_2}$)

(D) Various Combinations

Ex

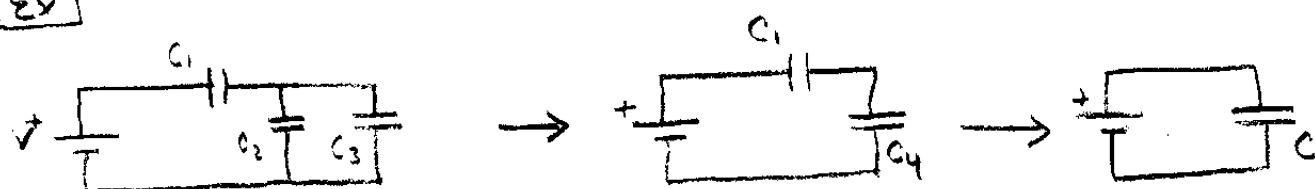

$$C_4 = C_2 \parallel C_3$$

$$= C_2 + C_3$$


$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_4}$$

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2 + C_3}$$

$$\frac{1}{C} = \frac{C_1 + C_2 + C_3}{C_1(C_2 + C_3)}$$

$$C = \frac{C_1(C_2 + C_3)}{C_1 + C_2 + C_3}$$

Ex

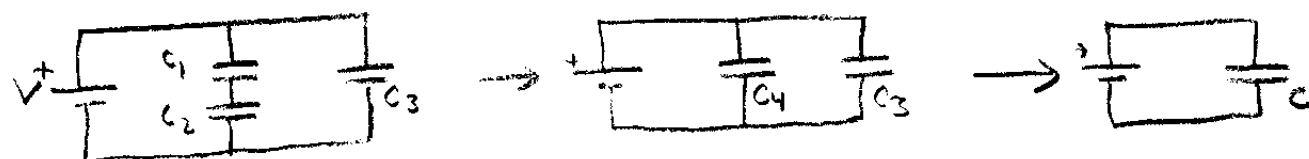

$$\frac{1}{C_4} = \frac{1}{C_1} + \frac{1}{C_2}$$


$$C = C_3 + C_4$$

$$C_4 = \frac{C_1 C_2}{C_1 + C_2}$$

$$C = C_3 + \frac{C_1 C_2}{C_1 + C_2}$$

$$C = \frac{C_3(C_1 + C_2) + C_1 C_2}{C_1 + C_2}$$

III. ENERGY STORED IN CAPACITORS

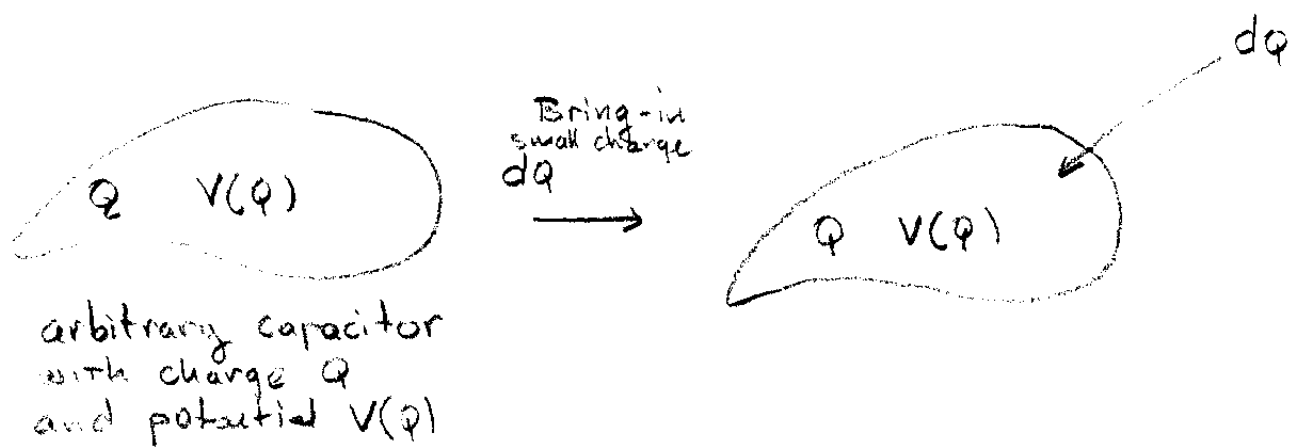

- Work done on system by bringing in charge dq to system is

$$dW = V(Q) dq$$

but $C = \frac{dQ}{dV}$

$$dq = C dV$$

$$dW = C V dV$$

$$\Delta W = \int dW = C \int V dV = \frac{1}{2} C V^2$$

$$\boxed{E_c = \frac{1}{2} C V^2}$$


Energy stored in capacitor C at voltage V

OR, since $C = \frac{Q}{V}$

$$E_c = \frac{1}{2} Q V$$

$$E_c = \frac{1}{2} \frac{Q^2}{C}$$

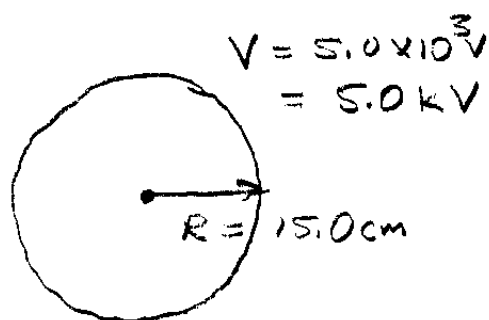EX: ENERGY STORED ON VAN DE GRAEFF GENERATOR



$$E = \frac{1}{2} CV^2$$

$$C = 4\pi\epsilon_0 R$$

$$E = 2\pi\epsilon_0 R V^2$$

$$= (2)(3.1415)(8.85 \times 10^{-12} \frac{C^2}{N \cdot m^2})(15.0 \times 10^{-2} m)(5.0 \times 10^3 \frac{J}{C})^2$$

$$E = 2.1 \times 10^{-4} J$$

Not much energy. This is why you didn't die when the Van de Graeff discharged through your body, even though its potential was up at 5.0 kV.

- Total Charge on sphere —

$$C = \frac{Q}{V} \Rightarrow Q = CV$$

$$= 4\pi\epsilon_0 R V$$

$$= (4)(3.1415)(8.85 \times 10^{-12} \frac{C^2}{N \cdot m^2})(15.0 \times 10^{-2} m) \times (5.0 \times 10^3 \frac{J}{C})$$

$$Q = 4.2 \times 10^{-8} C$$

$$Q = .42 nC$$

Really small amount of charge.