
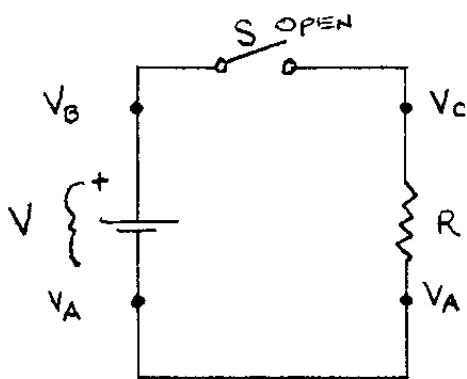


I. VOLTAGE DROPS AND RISES

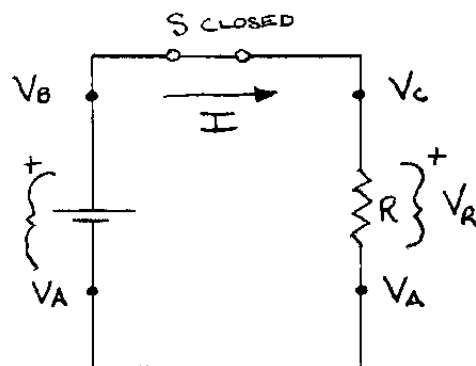

$$V_A + V = V_B$$

$$V_C = V_A$$



$$V_A + V - V_R = V_A$$

$$V - V_R = 0$$

$$V - IR = 0$$

$$V = IR \quad (\text{JUST OHM'S LAW})$$

Ex: $V = 9.0 \text{ V}$ (ideal battery)

$$R = 5.0 \Omega$$

$$I = \frac{V}{R}$$

$$= \frac{(9.0 \text{ V})}{(5.0 \Omega)}$$


$$= 1.8 \text{ A}$$

Ex: 9.0 V ALKALINE CELL CAN DELIVER ABOUT 1000 mA·hr OF CHARGE BEFORE ITS ALL USED-UP (i.e., 1000 mA for 1 hr, OR 500 mA for 2 hrs, etc.).

$$(1.8 \text{ A}) \left(\frac{1 \text{ BATTERY}}{1 \text{ A} \cdot \text{hr}} \right) = 1.8 \text{ BATTERIES/hr}$$

→ ABOVE BATTERY IS DEAD IN $\frac{1}{1.8} \text{ hrs} = 33 \text{ min!}$

II. ENERGY & POWER

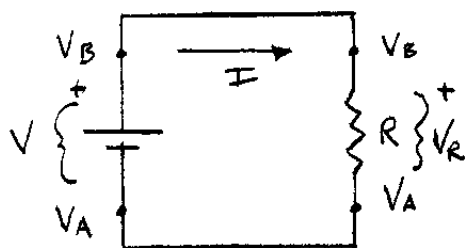

CHANGE IN POTENTIAL ENERGY
OF CHARGE q MOVING THROUGH
 R FROM POTENTIAL V_B TO
POTENTIAL V_A -

$$\Delta W = q \Delta V$$

$$(W_A - W_B) = q (V_A - V_B)$$

Choosing $W_A = V_A = 0$ (arbitrary - we can do this)
 $-W_B = q (-V_B)$

OR SIMPLY $W = qV$

$$[\text{POWER}] \equiv \left[\frac{\text{ENERGY}}{\text{UNIT TIME}} \right]$$

$$P = \frac{dW}{dt} \quad (\text{e.g., 1 Watt} = 1 \text{ J/sec})$$

$$P = \frac{dW}{dt} = \frac{dq}{dt} V + q \frac{dV}{dt}$$

Have $V = \text{const.}$ here, so $\frac{dV}{dt} = 0$

$$P = \frac{dq}{dt} V$$

$$\boxed{P = IV}$$

OR, SINCE

$$V = IR$$

$$\boxed{P = I^2 R}$$

$$\boxed{P = V^2 / R}$$

all three forms are
equivalent. Which one
you use is up to you.

Ex: POWER CONSUMPTION IN ABOVE EXAMPLE

KNOW: V & $R \Rightarrow$ QUICKEST TO USE

$$\begin{aligned} P &= V^2/R \\ &= (9.0V)^2/(5.0\Omega) \\ &= 16 \text{ Watts} \quad (J/s) \end{aligned}$$

BUT, SINCE WE ALSO WENT TO THE TROUBLE OF CALCULATING I

$$\begin{aligned} P &= IV \\ &= (1.8A)(9.0V) \\ &= 16 \text{ Watts} \end{aligned}$$


OR

$$\begin{aligned} P &= I^2 R \\ &= (1.8A)^2 (5.0\Omega) \\ &= 16 \text{ Watts} \end{aligned}$$

THIS ENERGY IS BEING SUPPLIED BY THE BATTERY. THE CHARGE-CARRIER COLLISIONS IN THE RESISTOR RESULT IN AN INCREASE OF KINETIC ENERGY OF THE MATERIAL, WHICH INCREASES ITS TEMPERATURE. THE ASSOCIATED HEAT IS DISSIPATED BY THE RESISTOR BY CONDUCTION/CONVECTION/RADIATION. THIS IS CALLED

JOULE HEATING

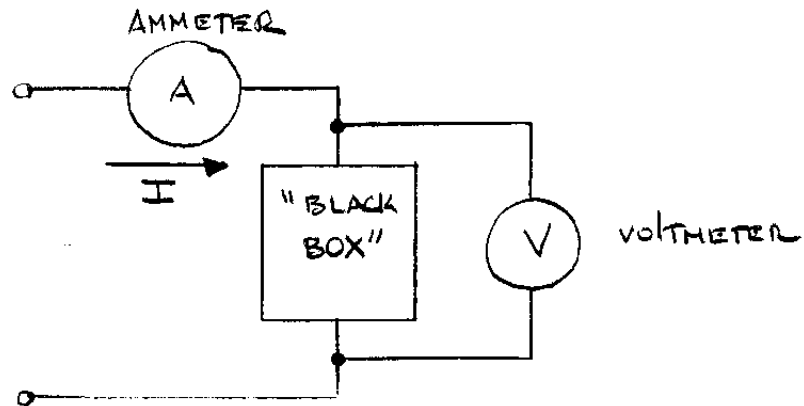NOTE THAT THE $P = IV$ RELATIONSHIP
ALLOWS ONE TO DETERMINE THE POWER
CONSUMPTION OF ANY CIRCUIT SIMPLY
BY MEASURING THE VOLTAGE ACROSS IT
AND THE CURRENT THROUGH IT



$P = IV$, REGARDLESS OF WHAT'S IN
THE "BLACK BOX".



III. CURRENT DENSITY AND CONDUCTIVITY

CHARGE IN AN ELECTRIC FIELD EXPERIENCES A FORCE

$$\vec{F} = q \vec{E}$$

AND THE CHARGE THEN MOVES ACCORDING TO THIS FORCE.

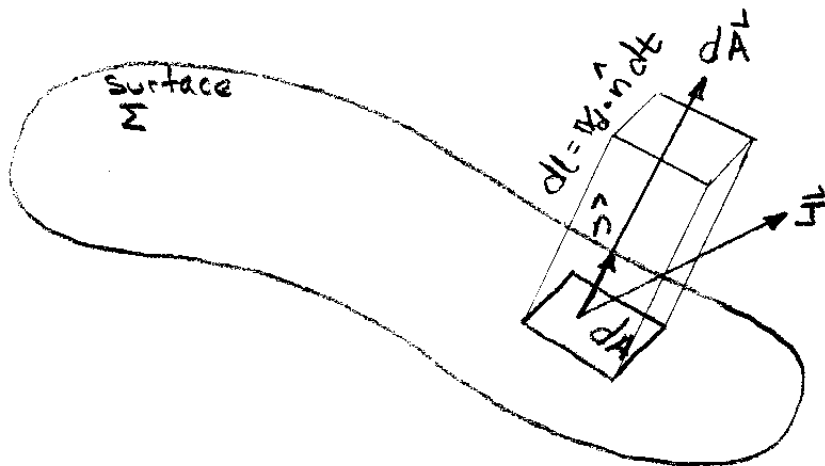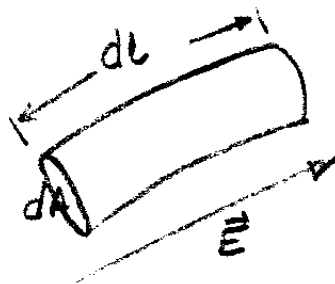IT IS THE ELECTRIC FIELD $\vec{E}$ THAT DETERMINES WHAT'S GOING TO HAPPEN (AND OF COURSE THE CHARGE EXPERIENCING IT), SO IT SHOULDN'T BE SURPRISING THAT THE CURRENT AT SOME POINT IN SPACE DEPENDS ULTIMATELY ON THE ELECTRIC FIELD THERE



$$I = \frac{dq}{dt} \quad \text{crossing some surface}$$

$$dI = \frac{dq}{dt} \quad \text{crossing some surface area element } dA$$

$$\begin{aligned} dI &= \left(\frac{dq}{dVol} \right) \left(\frac{dVol}{dt} \right) \\ &= \left(\frac{dq}{dVol} \right) \left(\frac{dl}{dt} \right) dA \\ &= \left(\frac{dq}{dVol} \right) (\mathbf{v}_d \cdot \hat{n}) dA \\ &= \underbrace{\left[\left(\frac{dq}{dVol} \right) \mathbf{v}_d \right]}_{\mathbf{J}} \cdot (\hat{n} dA) \end{aligned}$$

$$dI = \mathbf{J} \cdot d\vec{A}$$

Total current through entire surface Σ is

$$I = \int dI$$

$$I = \int_{\Sigma} \mathbf{J} \cdot d\vec{A}$$

FOR LINEAR MATERIALS AND $\vec{E}$ -FIELDS NOT TOO LARGE, IT TURNS OUT THAT

$$\vec{J} \sim \vec{E}$$

i.e.,

$$\vec{J} = \sigma \vec{E}$$

σ IS CALLED THE CONDUCTIVITY OF THE MATERIAL.

EX! FOR A SIMPLE RESISTOR

$$V = IR$$

$$V = I \frac{\rho L}{A}$$

$$EL = (\sigma EA) \frac{\rho L}{A}$$

$$1 = \sigma \rho$$



$$\Rightarrow \sigma = \frac{1}{\rho}$$

σ = conductivity

ρ = resistivity

Can be taken as a general definition.

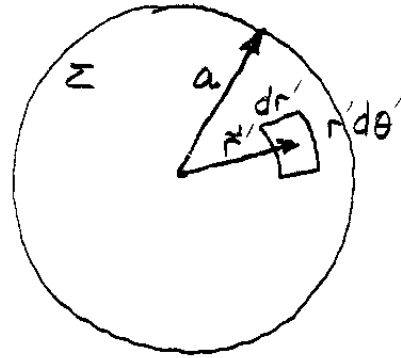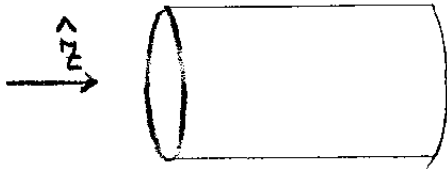Ex: NONUNIFORM ELECTRIC FIELD IN RESISTOR
(MORE REALISTIC) $E(r) = Kr$



$$I(r) = \int \vec{J}(r) \cdot d\vec{A}(r)$$

$$\vec{J}(r) = \sigma \vec{E}(r)$$

$$= \sigma K E(r) \hat{z}$$

$$d\vec{A}(r) = dA \hat{z} = r dr d\theta \hat{z}$$

$$I(r) = \int_0^r dr' \int_0^{2\pi} d\theta' (\sigma K r' \hat{z}) \cdot (r' \hat{z})$$

$$= \int_0^r dr' \int_0^{2\pi} d\theta' \sigma K r'^2$$

$$= 2\pi \sigma K \int_0^r dr' r'^2$$

$$I(r) = \frac{2\pi \sigma K}{3} r^3$$

$$\frac{dI(r)}{dr} = 2\pi \sigma K r^2$$

