
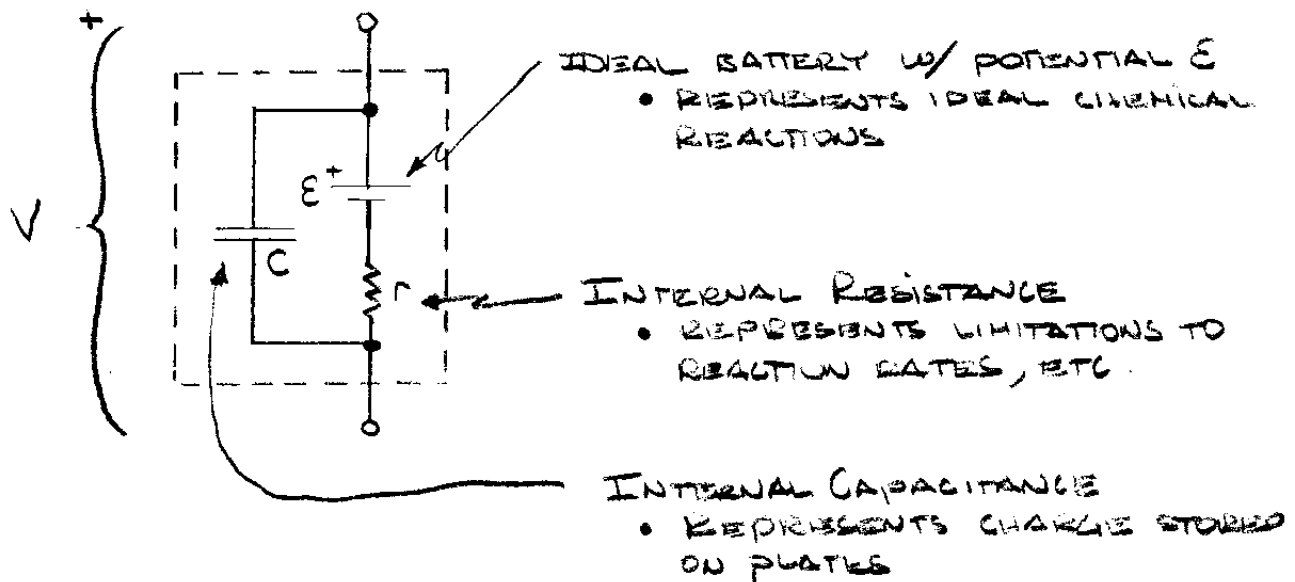


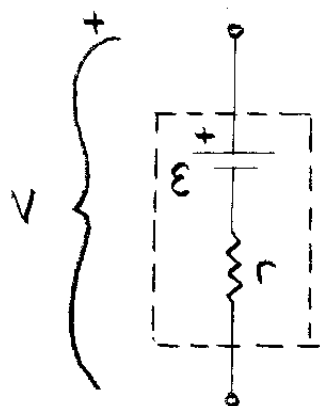I. REAL BATTERIES

UNLIKE THE IDEAL BATTERIES WE'VE CONSIDERED SO FAR, REAL BATTERIES HAVE INTERNAL RESISTANCE AND CAPACITANCE WHICH GREATLY ALTERS THEIR BEHAVIOR IN ACTUAL CIRCUITS



WE'LL NOT CONSIDER C HERE, JUST r




ϵ = OPEN-CIRCUIT VOLTAGE
(NO-LOAD, IDEAL BATTERY)

V = TERMINAL VOLTAGE

r = INTERNAL RESISTANCE

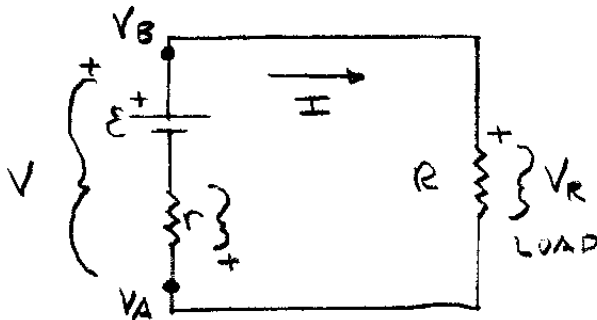- UNDER NO-LOAD CONDITIONS, NO CURRENT IS IN r , SO $V = \epsilon$



$$V_A - V_r + \mathcal{E} - V_R = V_A$$

$$\mathcal{E} - V_r - V_R = 0$$

$$\mathcal{E} - Ir - IR = 0$$

$$\mathcal{E} = I(r + R)$$

$$I = \mathcal{E} / (R + r)$$

- actual current supplied by battery under load is less than the ideal case of $I = \mathcal{E}/R$

$$V = V_B - V_A$$

$$= (V_A - Ir + \mathcal{E}) - (V_A)$$

$$V = \mathcal{E} - Ir$$


- actual voltage supplied by battery under load is less than ideal case of $V = \mathcal{E}$

$$V = \mathcal{E} - Ir$$

$$= \mathcal{E} - \frac{\mathcal{E}r}{(R+r)}$$

$$V = \frac{\mathcal{E}R}{(R+r)}$$

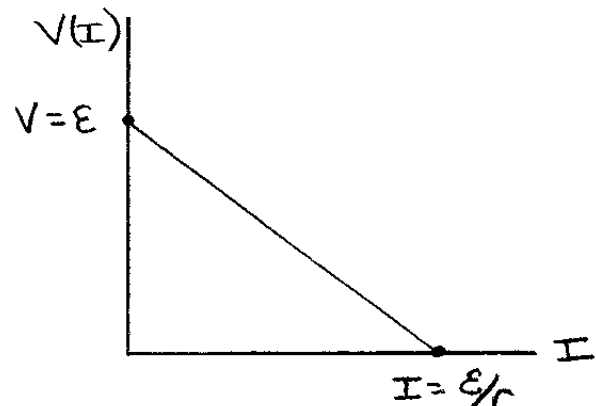- Voltmeters are actually useless by themselves to test whether a battery is good.




Ex: PUT A VOLTMETER ON AN OLD 9.0V BATTERY & PERHAPS GET $V = 9.0V$ READING.

BUT, INTERNAL RESISTANCE MAY BE AROUND 2.0Ω


HOOK THIS UP TO 5.0Ω LOAD -

- THINK YOU'LL GET
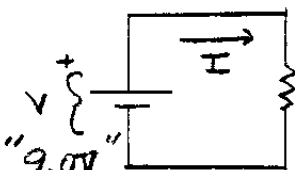
$$V - IR = 0$$


$$I = \frac{V}{R} = \frac{(9.0V)}{(5.0\Omega)} = 1.8A$$

- REALITY GET

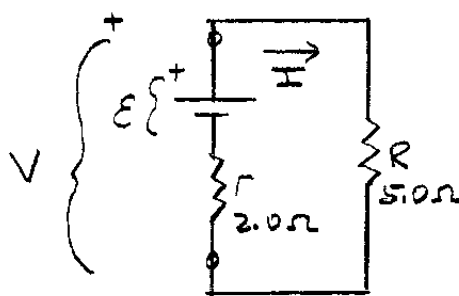

$$I = \frac{\epsilon}{(R+r)} = \frac{(9.0V)}{(8.0\Omega)} = 1.2A$$

$$V = \frac{\epsilon R}{(R+r)}$$


$$= \frac{(9.0V)(5.0\Omega)}{(5.0\Omega + 2.0\Omega)}$$

$$V = 5.6V$$

- This is what's really going on in your portable radio when it starts sounding lousy and needs a new battery - the actual voltage it's getting is dropping below the value it needs to work.

II. RESISTORS IN SERIES AND PARALLEL

(A) SERIES

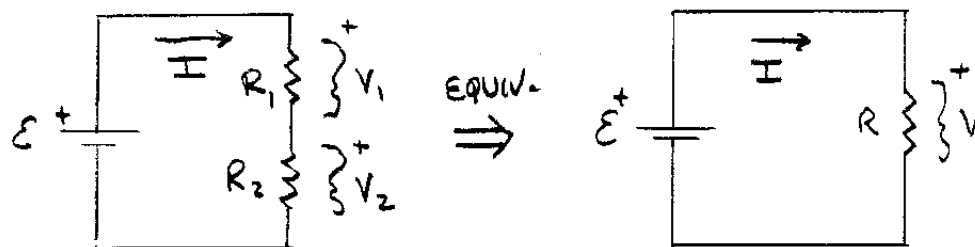

$$\mathcal{E} - V_1 - V_2 = 0$$

$$\mathcal{E} = V_1 + V_2$$

$$V = V_1 + V_2$$

$$IR = IR_1 + IR_2$$


$$R = R_1 + R_2$$

SERIES

$$\mathcal{E} - V_R = 0$$

$$\mathcal{E} = V$$

(B) PARALLEL

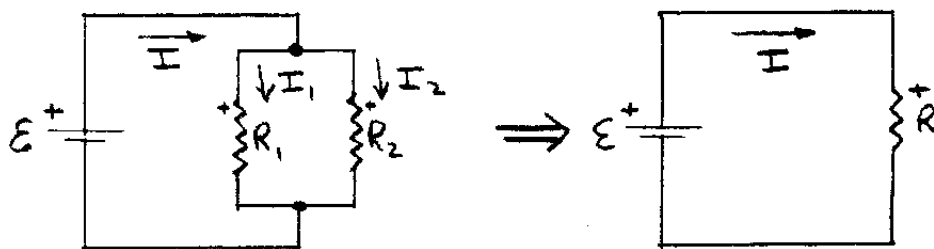

$$I - I_1 - I_2 = 0$$

$$I = I_1 + I_2$$


$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

PARALLEL

- Note: These relationships are just the "opposite" of those for capacitors

EX:

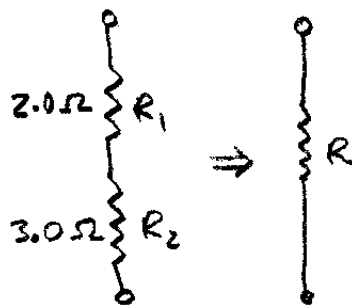


• SERIES

$$R = R_1 + R_2$$

$$= 2.0\Omega + 3.0\Omega$$

$$R = 5.0\Omega$$

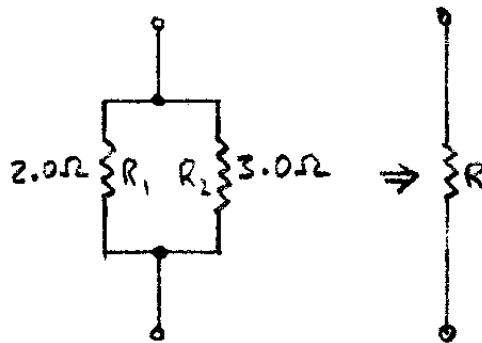- Equivalent Series resistance is always greater than greatest single resistance in series.



• PARALLEL


$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{(2.0\Omega)(3.0\Omega)}{(2.0\Omega + 3.0\Omega)}$$

$$R = 1.2\Omega$$

- Equivalent parallel resistance is always smaller than smallest single resistance in parallel.

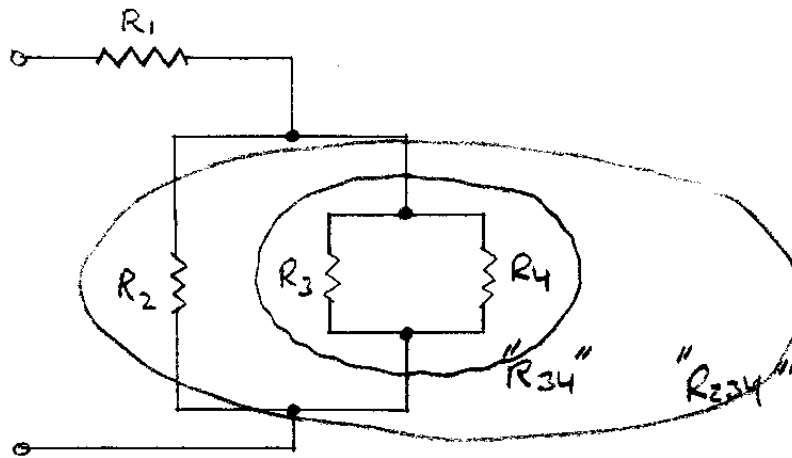EX! SERIES AND PARALLEL COMBOS


$$R_{34} = R_3 \parallel R_4 = \frac{R_3 R_4}{R_3 + R_4}$$

$$\begin{aligned} R_{234} &= R_2 \parallel (R_3 \parallel R_4) \\ &= \frac{R_2 (R_3 \parallel R_4)}{R_2 + (R_3 \parallel R_4)} \\ &= \frac{R_2 \left(\frac{R_3 R_4}{R_3 + R_4} \right)}{R_2 + \left(\frac{R_3 R_4}{R_3 + R_4} \right)} \end{aligned}$$

$$R_{eq} = R_{234} = R_1 + R_{234}$$

$$R = R_1 + \frac{R_2 \left(\frac{R_3 R_4}{R_3 + R_4} \right)}{R_2 + \left(\frac{R_3 R_4}{R_3 + R_4} \right)}$$

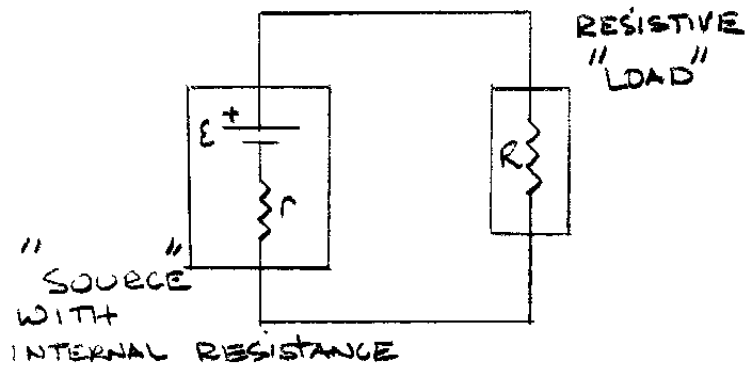III. POWER TRANSFER IN RESISTIVE CIRCUITS



POWER TRANSFER FROM SOURCE TO LOAD

$$P = I^2 R$$

$$I = \mathcal{E} / (R + r)$$

$$P = \frac{\mathcal{E}^2 R}{(R + r)^2}$$


Maximum power transfer occurs at

$$\frac{\partial P}{\partial R} = 0$$

$$\frac{\partial P}{\partial R} = \mathcal{E}^2 \left[\frac{(R+r)^2(1) - (2)(R)(R+r)}{(R+r)^4} \right]$$


$$= \frac{2\mathcal{E}^2(r-R)}{(R+r)^3} = 0 \text{ for } r = R$$
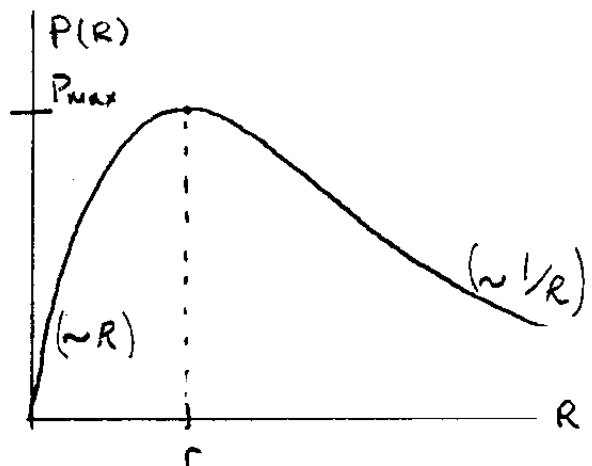
$$P_{\max} = \frac{\mathcal{E}^2 R}{(R+R)^2} = \frac{1}{4} \mathcal{E}^2 / R$$



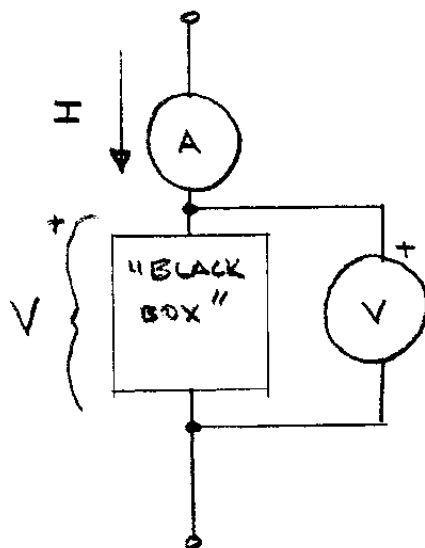
IV. AMMETERS AND VOLTMETERS

- AN IDEAL AMMETER WOULD TELL YOU EXACTLY WHAT CURRENT YOU HAVE THROUGH SOME CIRCUIT WITHOUT CAUSING ANY CHANGE TO THE CURRENT MEASURED.
- AN IDEAL VOLTMETER WOULD TELL YOU EXACTLY WHAT VOLTAGE YOU HAVE ACROSS SOME CIRCUIT WITHOUT CAUSING ANY CHANGE TO THE VOLTAGE MEASURED.



- IDEAL AMMETER READS EXACTLY I
- IDEAL VOLTMETER READS EXACTLY V
- THEY HAVE NO AFFECT ON THE CIRCUIT.

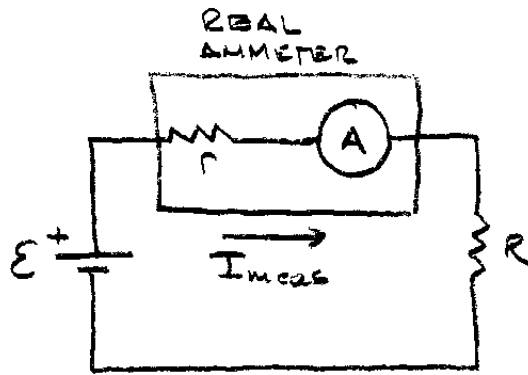- OF COURSE, REAL VOLTMETERS AND AMMETERS ARE THEMSELVES ELECTRONIC DEVICES, AND THEY HAVE INTERNAL RESISTANCES ALL THEIR OWN. HOOKING THEM UP TO A CIRCUIT ACTUALLY CHANGES THE CIRCUIT, SO VOLTAGES AND CURRENTS BEING MEASURED ARE NOT THE SAME AS WITHOUT THE INSTRUMENTS ATTACHED.




$$\varepsilon - I_{\text{meas}} r - I_{\text{meas}} R = 0$$

$$\varepsilon = I_{\text{meas}} (R + r)$$

$$I_{\text{meas}} = \frac{\varepsilon}{(R + r)}$$

$$= \frac{(\varepsilon/R)}{1 + (r/R)}$$
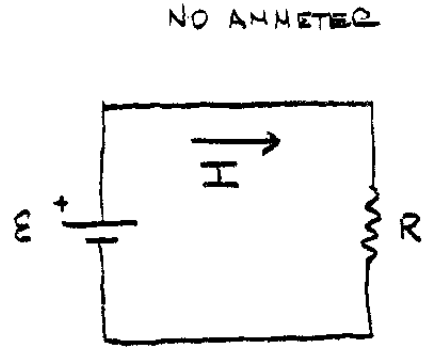
$$I_{\text{meas}} = \frac{I}{1 + (r/R)}$$



$$\varepsilon - IR = 0$$

$$\varepsilon = IR$$

$$I = \frac{\varepsilon}{R}$$

- Want to have $I_{\text{meas}} = I$, but this requires $r/R = 0$ (or, $r = 0$, which is not possible). Best one can do is to try to get r/R as small as possible (takes very expensive ammeters to accurately measure small resistances!)