
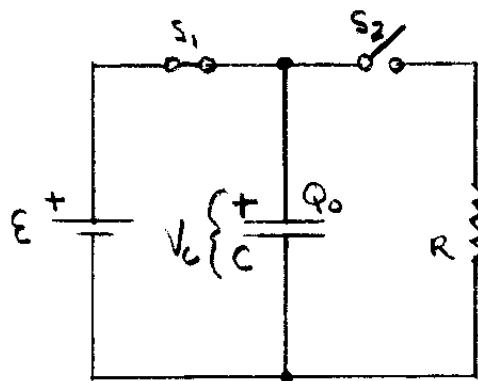


I. RC CIRCUITS

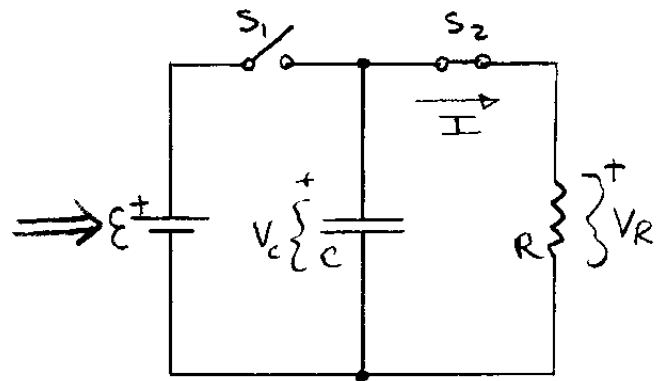

Capacitor C charged
by battery to $V_C = \mathcal{E}$
 $Q = Q_0$



Capacitor discharged
through resistor R

Switch S_1 opened $\Rightarrow V_C - V_R = 0$
Then S_2 closed $V_C = V_R$

$$V_C = Q/C$$

$$V_R = IR$$

$$IR = Q/C$$

$$\text{BUT } I = -dQ/dt$$

(-) because charge
is leaving in
direction shown

$$R \frac{dQ}{dt} = -\frac{Q}{C}$$

$$\frac{dQ}{dt} = -\frac{1}{RC} Q$$

$$\frac{dQ}{Q} = -\frac{1}{RC} dt$$

$$\int \frac{dQ}{Q} = -\frac{1}{RC} \int dt$$

$$\ln|Q| = -t/RC + \text{const.}$$

$$Q(t) = e^{-t/RC} e^{\text{const.}}$$


$$Q(t) = A e^{-t/RC}$$

$$(A \equiv e^{\text{const.}})$$

$$Q(0) = Q_0 = EC$$

$$\Rightarrow A = EC$$

$$Q(t) = EC e^{-t/RC}$$

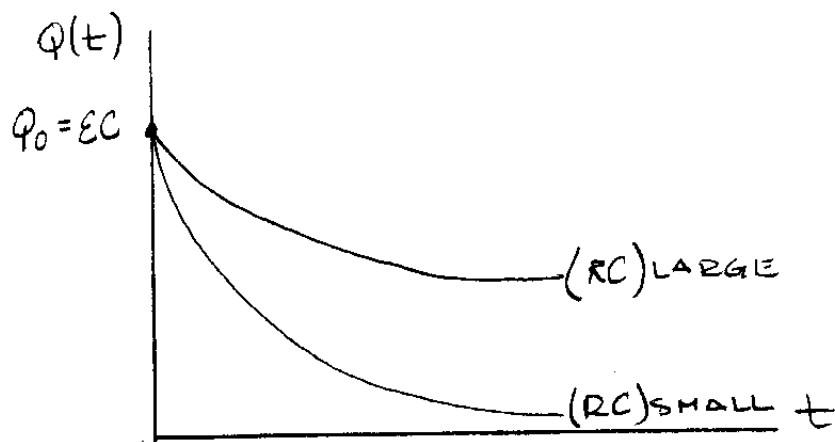

- "RC TIME CONSTANT"

NOTE THAT THE LARGER (RC) IS, THE LONGER IT TAKES FOR AN RC CIRCUIT TO CHARGE (OR DISCHARGE).

LOOK AT THE UNITS OF RC -

$$\begin{aligned} RC &= (\Omega) \cdot (F) \\ &= \left(\frac{V}{A} \right) \cdot \left(\frac{C}{V} \right) \\ &= \frac{C}{A/s} \end{aligned}$$

RC $\Rightarrow$ sec. IT HAS DIMENSIONS OF TIME (AS IT SHOULD, SINCE $e^{-t/RC}$ MUST HAVE A DIMENSIONLESS, i.e., TIME/TIME, exponent)

DEFINE

$$\tau_0 \equiv RC$$

"RC TIME CONSTANT"

WHAT HAPPENS IF $t = \tau_0$?


$$\begin{aligned} Q(t) &= EC e^{-t/RC} \\ &= EC e^{-t/\tau_0} \end{aligned}$$

$$Q(\tau_0) = EC e^{-1}$$

$$Q(\tau_0) = e^{-1} Q_0$$

τ_0 SAYS HOW LONG IT WILL TAKE FOR THE CAPACITOR TO DISCHARGE (CHARGE) TO $\frac{1}{e}$ OF ITS ORIGINAL CHARGE.

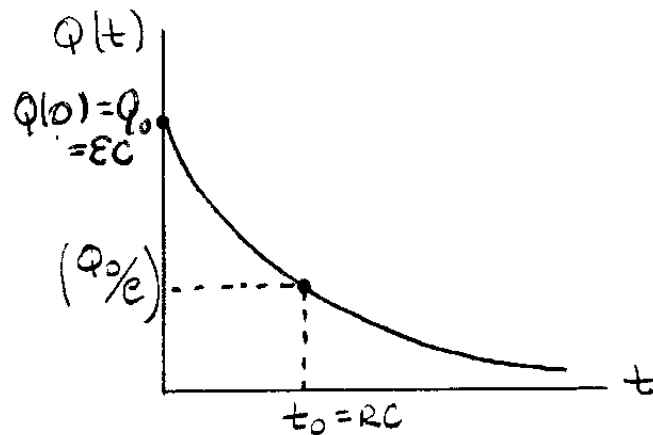(*NOTE: DON'T CONFUSE THIS $e \approx 2.718$
WITH THE OTHER $e = 1.602 \times 10^{-19} \text{ C}$!
This e is just $\ln(e) \equiv 1$)



Ex: FOR ABOVE CIRCUIT WITH $R = 2.5 \Omega$, $C = 5.0 \mu\text{F}$

$$t_0 = RC$$

$$= (2.5 \Omega)(5.0 \mu\text{F})$$

$$t_0 = 13 \mu\text{s}$$


Takes $13 \mu\text{s}$ for capacitor to discharge to $\frac{1}{e} \approx 0.3679$ of its original charge.


• The voltage: $V(t) = Q(t)/C$

$$V(t) = \frac{Q_0}{C} e^{-t/RC}$$

$$= \frac{EC}{C} e^{-t/RC}$$

$$V(t) = E e^{-t/RC}$$

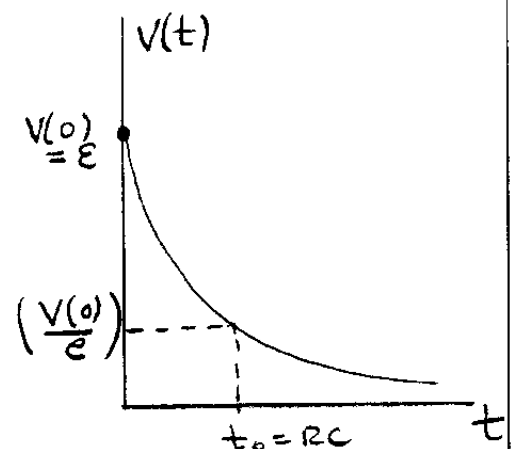

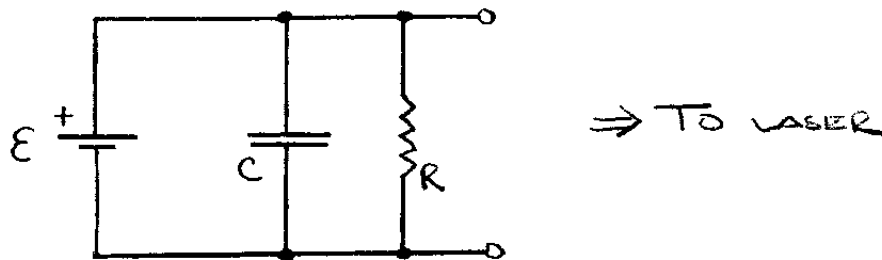Ex! Typ. LASER POWER SUPPLY

$$\epsilon = 5000 \text{ V}, \quad C = 1.0 \times 10^{-3} \text{ F}, \quad R = 1.0 \text{ M}\Omega.$$

C IS MEANT TO SUPPLY THE HIGH-CURRENT BURSTS NEEDED BY LASER.

R IS MEANT TO SLOWLY DISCHARGE C WHEN SUPPLY NOT IN-USE (TO MAKE IT "SAFE")

$$t_0 = RC$$

$$= (1.0 \times 10^6 \Omega)(1.0 \times 10^{-3} \text{ F})$$

$$= 1.0 \times 10^3 \text{ sec} = 17 \text{ min to discharge to } \frac{1}{e} \text{ of } 5000 \text{ V} = 1.8 \times 10^3 \text{ V}$$

Ex! PHYSICS GRAD STUDENT UNPLUGS LASER POWER SUPPLY, GETS COVER OFF WITHIN 1 MIN, & STICKS SCREWDRIVER IN

$$V(t) = V_0 e^{-t/RC}$$


$$V(t=60 \text{ sec}) = (5000 \text{ V}) e^{-\left(\frac{60 \text{ sec}}{1.0 \times 10^3 \text{ sec}}\right)}$$

$$V(t=60 \text{ sec}) = 4700 \text{ Volts}$$

INSTANT GUEST-OF-HONOR AT DIOS DE LOS MUERTOS PARADE!

LESSON: JUST BECAUSE YOU SHUT-OFF A POWER SUPPLY DOESN'T MEAN IT WON'T KILL YOU!!

• ANOTHER CIRCUIT

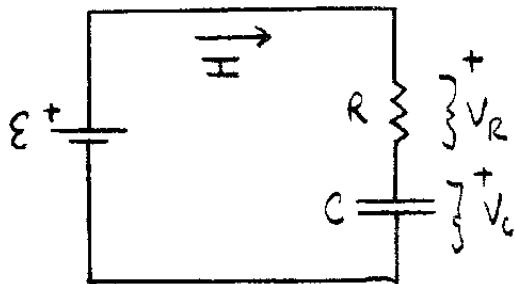

$$\varepsilon - V_R - V_C = 0$$

$$\varepsilon - IR - Q/C = 0$$

$$I = dQ/dt$$

$$\varepsilon - R \frac{dQ}{dt} - \frac{Q}{C} = 0$$

$$R \frac{dQ}{dt} + \frac{Q}{C} = \varepsilon$$

$$\frac{dQ}{dt} + \frac{1}{RC} Q = (\varepsilon/R)$$

$$\frac{dQ}{dt} = (\varepsilon/R) - (\frac{1}{RC}) Q$$

$$\frac{dQ}{(\varepsilon/R) - (\frac{1}{RC}) Q} = dt \Rightarrow \frac{dQ}{(\frac{1}{RC}) - (\frac{\varepsilon}{R})} = -dt$$

$$\frac{dQ}{Q - (\varepsilon C)} = -\frac{1}{RC} dt \Rightarrow \int \frac{dQ}{Q - (\varepsilon C)} = -\frac{1}{RC} \int dt$$

$$\ln |Q - (\varepsilon C)| = -t/RC + \text{const.}$$

$$Q - (\varepsilon C) = A e^{-t/RC}$$

$$Q(t) = \varepsilon C + A e^{-t/RC}$$

$$\text{let } Q(0) = Q_0 \Rightarrow \varepsilon C + A = Q_0 \Rightarrow A = (Q_0 - \varepsilon C)$$


$$Q(t) = \varepsilon C + (Q_0 - \varepsilon C) e^{-t/RC}$$

$$\text{For } Q(0) = Q_0 = 0,$$

$$Q(t) = \varepsilon C (1 - e^{-t/RC})$$


- FOR ABOVE CIRCUIT (WITH $Q(0) = Q_0 = 0$)

- $Q(t) = \epsilon C (1 - e^{-t/RC})$

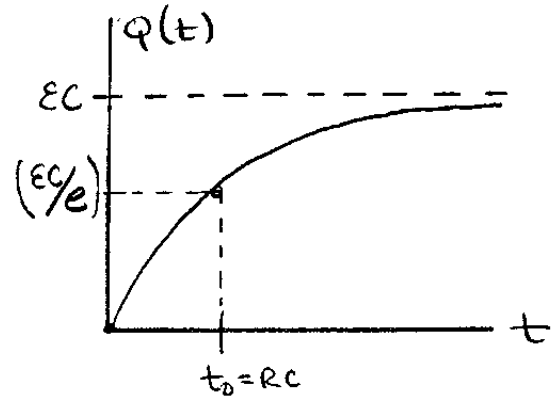


- $I(t) = \frac{dQ(t)}{dt}$
 $= \epsilon C \left(\frac{1}{RC} e^{-t/RC} \right)$

$$I(t) = \frac{\epsilon}{R} e^{-t/RC}$$

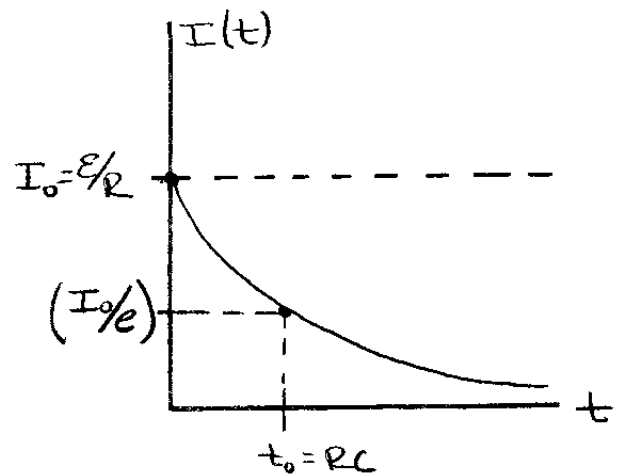

- $V(t) = Q(t)/C$

$$V(t) = \epsilon (1 - e^{-t/RC})$$

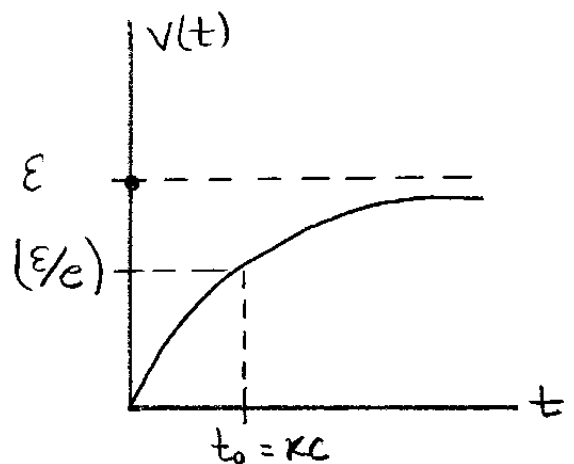

II. NETWORK ANALYSIS / KIRCHOFF'S RULES

(A) KIRCHOFF'S RULES

(1) LOOP RULE ("KLR")


$$\left(\sum_{\text{closed loop}} V_i = 0 \right)$$

- SUM OF ALL VOLTAGE DROPS/RISES THROUGH ANY CLOSED LOOP IS ZERO.

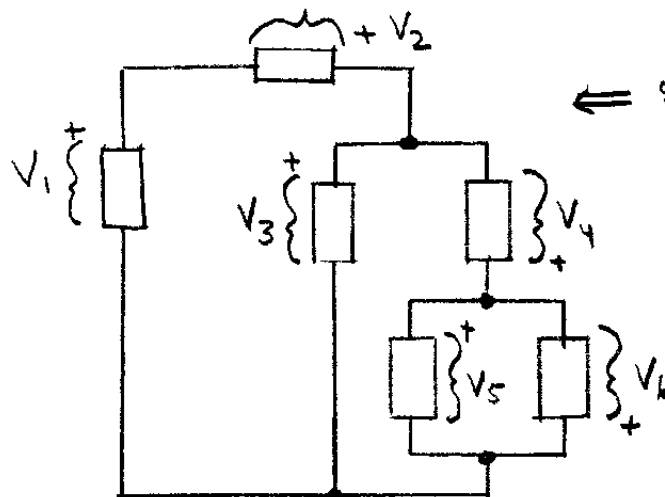(2) NODE RULE ("KNR")

$$\left(\sum_{\text{node}} I_i = 0 \right)$$

- SUM OF ALL CURRENTS ENTERING/LEAVING A NODE IS ZERO.




← SOME WHACKY CIRCUIT

- "KLR": ① $V_1 + V_2 - V_3 = 0$
 ② $V_1 + V_2 + V_4 - V_5 = 0$
 ③ $V_1 + V_2 + V_4 + V_6 = 0$
 ④ $V_3 + V_4 - V_5 = 0$
 ⑤ $V_3 + V_4 + V_6 = 0$
 ⑥ $V_5 + V_6 = 0$

- Any closed loop you go-around most return you to the same potential you started at!


"KNR"

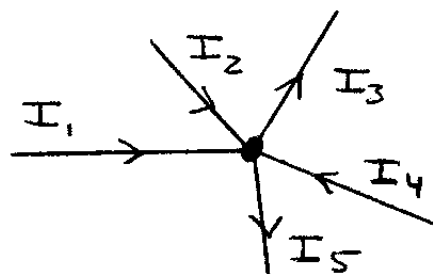

← SOME WHACKY
NODE WITH
FIVE CURRENTS
ENTERING / LEAVING

$$I_1 + I_2 - I_3 + I_4 - I_5 = 0 \quad (\text{etc}).$$

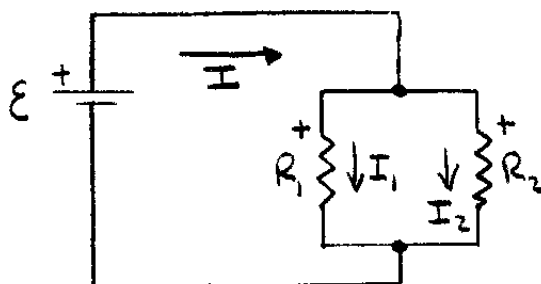EX1 SEEN BEFORE. NOW THROUGH KIRCHOFF'S EYES—




$$\begin{aligned} \textcircled{1} \text{ "KLR": } & \left. \begin{aligned} E - I_1 R_1 &= 0 \\ E - I_2 R_2 &= 0 \end{aligned} \right\} \begin{aligned} &3 \text{ eqns.} \\ &3 \text{ unks } (I, I_1, I_2) \end{aligned} \\ \text{"KNR": } & I - I_1 - I_2 = 0 \end{aligned} \Rightarrow \text{guaranteed a unique solution}$$

$$\begin{aligned} \textcircled{2} \text{ SOLVE: } & I_1 = E/R_1 \\ & I_2 = E/R_2 \\ & I - \frac{E}{R_1} - \frac{E}{R_2} = 0 \end{aligned}$$

$$\text{Just } \frac{E}{R_{eq}} = \frac{E}{R_1} + \frac{E}{R_2}$$

* Overkill : COULD HAVE JUST THOUGHT ABOUT IT FIRST, AND SOLVED AS BEFORE.

* LESSON : THINK FIRST

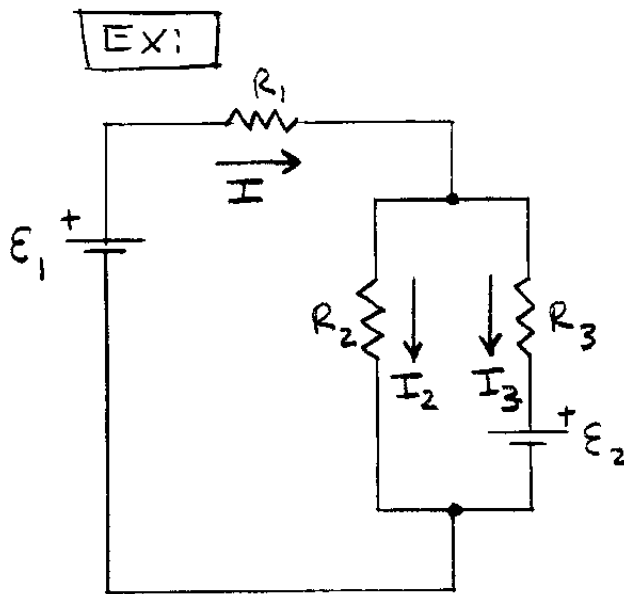

- NOT SO EASY TO SEE WHAT WILL HAPPEN. JUST PICK ANY DIRECTION FOR I , I_2 , & I_3
- ALL DEPENDS ON E_1 & E_2 .

$$\textcircled{1} \text{ "KLR": } E_1 - IR_1 - I_2 R_2 = 0 \quad \textcircled{1}$$

$$E_1 - IR_1 - I_3 R_3 - E_2 = 0 \quad \textcircled{2}$$

$$\textcircled{2} \text{ "KNR": } I - I_2 - I_3 = 0 \quad \textcircled{3}$$

Rearrange —

$$IR_1 + I_2 R_2 = E_1 \quad \textcircled{1}$$

$$IR_1 + I_3 R_3 = (E_1 - E_2) \quad \textcircled{2}$$

$$I_3 = I - I_2 \quad \textcircled{3}$$

SOLVE —

$$IR_1 + (I - I_2)R_3 = (E_1 - E_2) \quad \textcircled{4} \quad \left(\begin{array}{l} \text{SUBST } \textcircled{3} \\ \text{INTO } \textcircled{2} \end{array} \right)$$

$$I(R_1 + R_3) - I_2 R_3 = (E_1 - E_2)$$

$$IR_1 + I_2 R_2 = E_1 \quad \text{(JUST } \textcircled{1})$$

same
→

$$\left(\begin{array}{l} I \left(\frac{R_1 + R_3}{R_3} \right) - I_2 = \frac{(E_1 - E_2)}{R_3} \\ I R_1 / R_2 + I_2 = E_1 / R_2 \end{array} \right)$$

ADD EQNS TO ELIMINATE I_2 —

$$I \left(\frac{R_1}{R_2} + \left(\frac{R_1 + R_3}{R_3} \right) \right) = \frac{(\mathcal{E}_1 - \mathcal{E}_2)}{R_3} + \frac{\mathcal{E}_1}{R_2}$$

$$I \left[\frac{R_1 R_3 + (R_1 + R_3) R_2}{R_2 R_3} \right] = \frac{R_2 (\mathcal{E}_1 - \mathcal{E}_2) + \mathcal{E}_1 R_3}{R_2 R_3}$$

$$I = \frac{R_2 (\mathcal{E}_1 - \mathcal{E}_2) + \mathcal{E}_1 R_3}{R_2 R_3} \cdot \frac{R_2 R_3}{R_1 R_3 + (R_1 + R_3) R_2}$$

$$I = \frac{R_2 (\mathcal{E}_1 - \mathcal{E}_2) + \mathcal{E}_1 R_3}{R_1 R_3 + R_2 (R_1 + R_3)}$$

NOTICE THAT $I < 0$ FOR

$$R_2 (\mathcal{E}_1 - \mathcal{E}_2) + \mathcal{E}_1 R_3 < 0$$

OR

$$\mathcal{E}_2 > \mathcal{E}_1 \left(1 + R_3/R_2 \right)$$

THAT'S OKAY — IT JUST MEANS THAT THE CURRENT IS REALLY GOING IN A DIRECTION OPPOSITE TO WHAT YOU PICKED BEFORE YOU REALLY KNEW WHAT WAS GOING TO HAPPEN.

DON'T CHANGE YOUR ARROWS — IT'S UNDERSTOOD THAT A NEGATIVE VALUE FOR THEM JUST MEANS "THE OTHER WAY."

STRATEGY

- ① USE PHYSICAL REASONING FIRST. SIMPLE PROBLEMS CAN BE SOLVED BY SIMPLE MEANS, WITHOUT RESORT TO KIRCHOFF'S RULES.
- ② DEPENDING ON WHAT YOU WANT TO KNOW, SIMPLIFY CIRCUITS TO EQUIVALENT CIRCUITS (NO NEED TO ANSWER A QUESTION THAT IS NOT OF CONCERN.)
- ③ WHEN YOU CAN GO NO FARTHER WITH ① AND ②, RESORT TO THE "BRUTE-FORCE" OF KIRCHOFF'S RULES.

- (a) Arbitrarily assign current directions.
- (b) LABEL $\oplus$ SIDE OF VOLTAGE SOURCES, ETC.
- (c) Write-down Loop Eqs, "KLR".
- (d) Write-down Node Eqs, "KNR".
- (e) SOLVE your N-simultaneous Eqs for the N-unknowns.
- (f) Remember that negative values for currents only mean that the current is really in a direction opposite to that which you originally chose.